 


# Assignment - 1

Following the MOSEK setup on your python environment, the objective of the assignment is to find the  $T_{wall}$  and minimum area (under given timing specifications) of the circuit below



## 1. Finding $T_{wall}$ of the given circuit:

- Define the total number of gates in the circuit.
- Create Logical Effort and Parasitic Delay Lists
- Setup the Objective and Constraints to Minimize Timing
- Formulate the delay equation using logical effort and parasitic delay.
- Add constraints to ensure gate sizes remain within valid limits.
- Use GPkit to solve the optimization model.
- Extract the optimized gate sizes and report the total delay.

## 2. Optimize circuit for Minimum Area

- Change the objective function to minimize the total gate area instead of delay.
- Modify constraints to ensure timing meets a given timing specification.
- Solve the new model and report the optimized gate sizes for minimum area.

### Assumptions:

- Intrinsic delay of inverter is 5ps
- Maximum gate size of 64x and minimum size of 1x
- Capacitance at the end of the inverter chain (C) is 100 times the unit sized inverter
- Parasitic effort and logical effort values are ideal

### Deliverables:

- Report gate sizes for the circuit for optimized timing ( $T_{wall}$ )
- Report gate sizes for the area minimised circuit with a timing specification of  $1.2 \times T_{wall}$